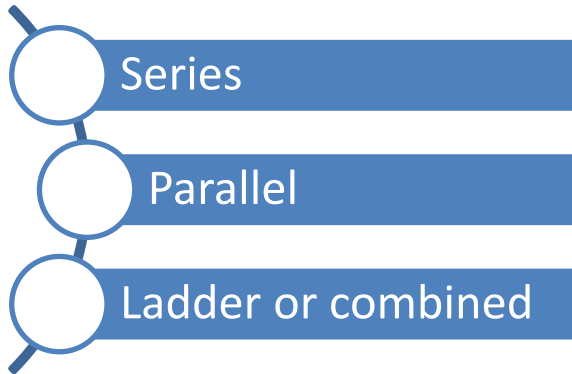


Topic 2


Equivalent resistance, voltage-current divider rule, delta-star transformations

Connections




Individual resistors can be connected together in either a series connection, a parallel connection or combinations of both series and parallel, to produce more complex resistor networks whose equivalent resistance is the mathematical combination of the individual resistors connected together.

Series Connection

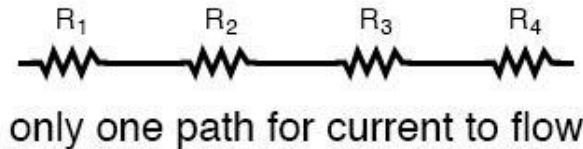

Parallel Connection

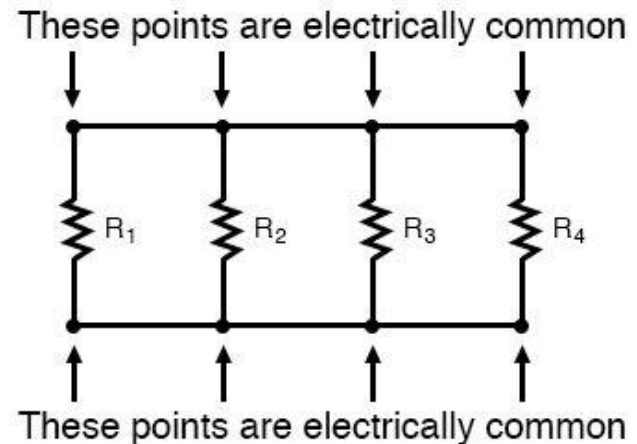

- ✚ In a series circuit, all components are connected end-to-end, forming a single path for current flow.
- ✚ In a parallel circuit, all components are connected across each other, forming exactly two sets of electrically common points.

Series Connection

Equivalent resistance, $R_T = R_1 + R_2 + R_3 + \dots + R_n$

Example:

Equivalent resistance for the series arrangement (fig. a),

$$R_T = R_1 + R_2 + R_3$$


$$R_T = 15 + 20 + 15 = 50 \Omega$$

$$I = E/R_T = 14/50 = 0.28 \text{ A} \quad (\text{applying Ohm's Law})$$

$$V_1 = IR_1 = 0.28 \times 15 = 4.2 \text{ V} \quad (\text{applying Ohm's Law})$$

$$V_2 = IR_2 = 0.28 \times 20 = 5.6 \text{ V} \quad (\text{applying Ohm's Law})$$
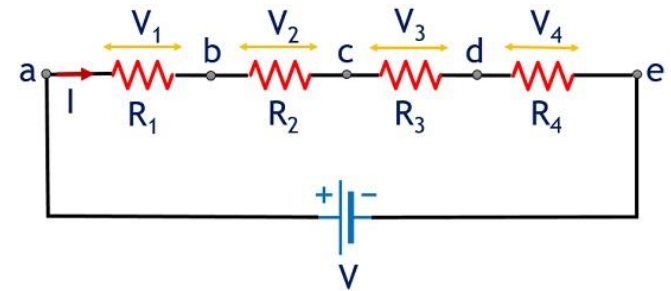
$$V_3 = IR_3 = 0.28 \times 15 = 4.2 \text{ V} \quad (\text{applying Ohm's Law})$$



Series Circuit

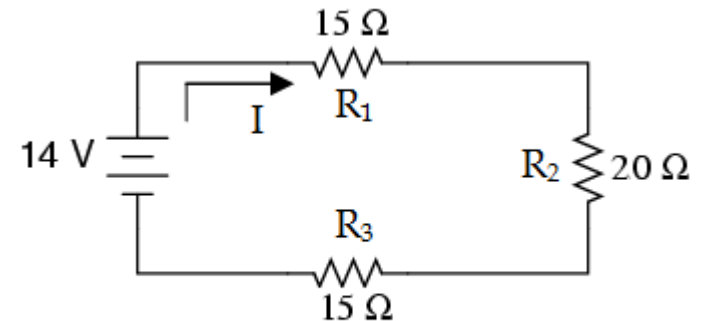


Figure: (a)

Parallel Connection

Equivalent resistance, $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$

Example:


Equivalent resistance for the parallel arrangement (fig. b),

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{3} + \frac{1}{6} = \frac{6+10+5}{30} = \frac{21}{30}$$

$$R_T = \frac{30}{21} = 1.43\Omega$$

$$I = E/R_T = 20/1.43 = 14 \text{ A}$$

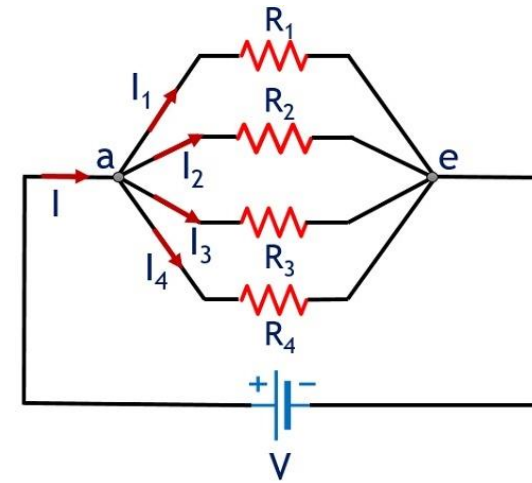

Parallel Circuit

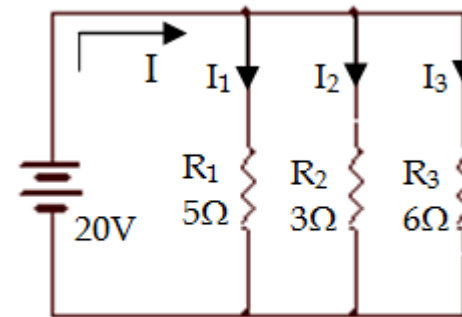


Figure: (b)

Series-Parallel Connection

Example:

Equivalent resistance for the series - parallel arrangement (fig. c),

$$R_T = R_1 + R_2 \parallel R_3 = 4\Omega + 2\Omega \parallel 1\Omega = 4 + 0.67 = 4.67\Omega$$



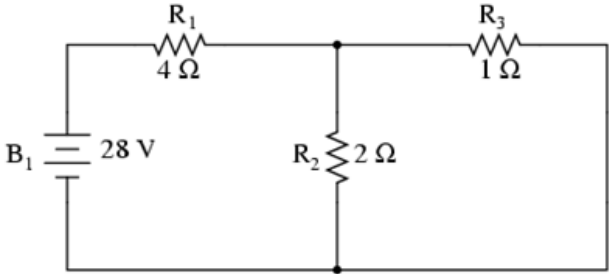
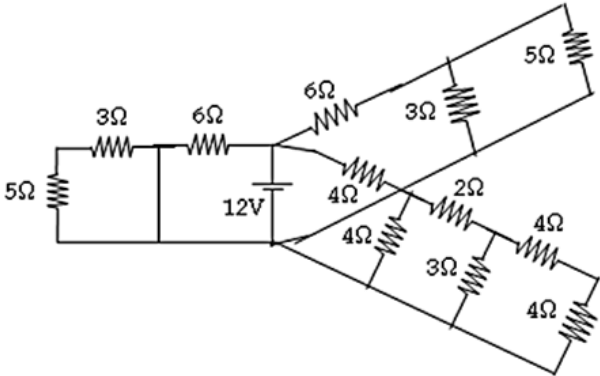
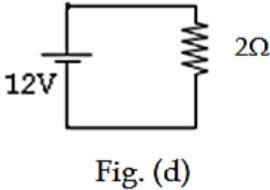
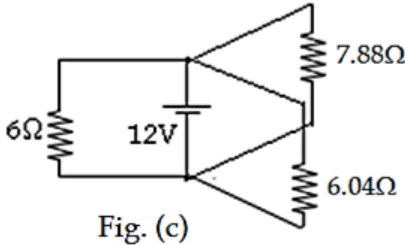


Figure: (c)


Problem 1: Calculate the equivalent resistance of the following circuit shown below,

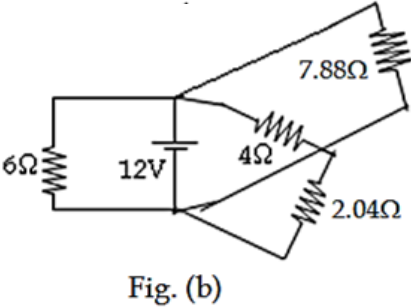

Solution 1:

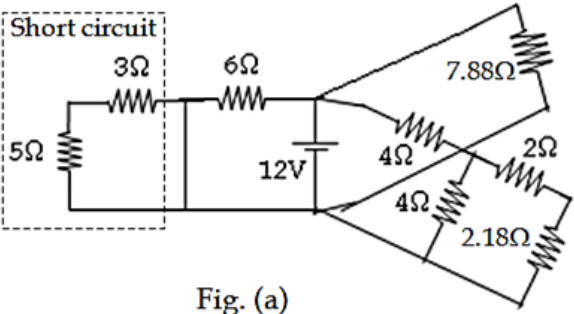

Problem 2: Calculate the equivalent resistance of the following circuit shown below,

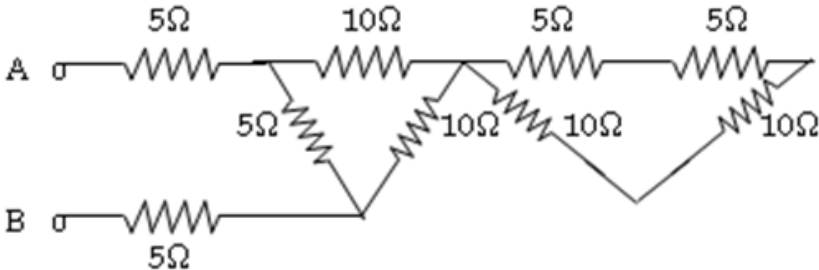

Solution 2:

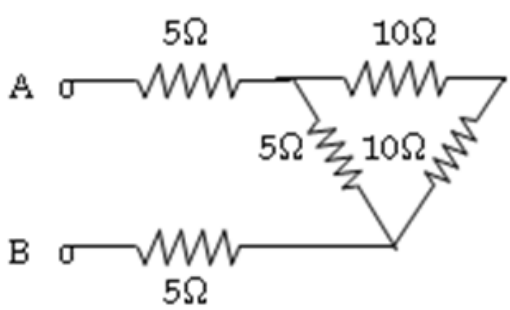
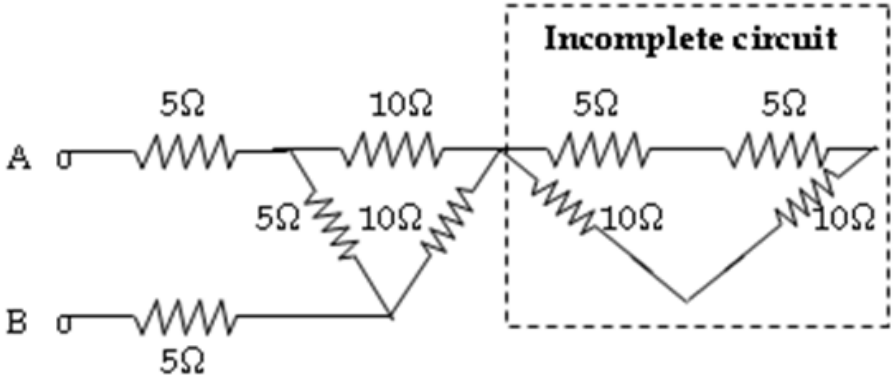


Fig. (a)

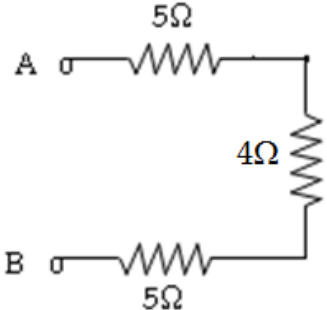


Fig. (b)

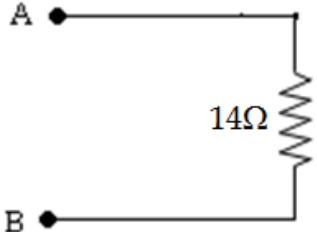


Fig. (c)

Voltage-Current divider rule

VOLTAGE DIVIDER RULE:

In fig. (a),

$$V_1 = \frac{E \times R_1}{R_1 + R_2 + R_3} = \frac{14 \times 15}{15 + 20 + 15} = \frac{210}{50} = 4.2V$$

$$V_2 = \frac{E \times R_2}{R_1 + R_2 + R_3} = \frac{14 \times 20}{15 + 20 + 15} = \frac{280}{50} = 5.6V$$

$$V_3 = \frac{E \times R_3}{R_1 + R_2 + R_3} = \frac{14 \times 15}{15 + 20 + 15} = \frac{210}{50} = 4.2V$$

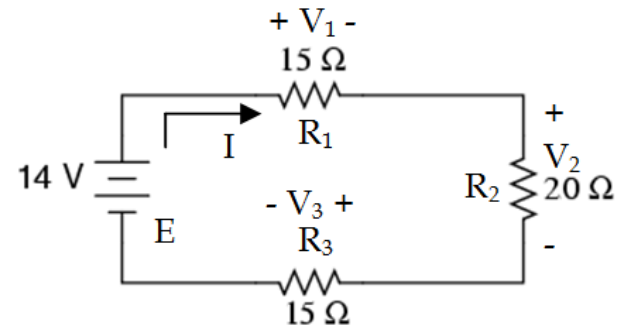


Figure: (a)

CURRENT DIVIDER RULE:

In fig. (b),

$$R_T = R_1 \parallel R_2 = 5 \parallel 7 = 2.92\Omega$$

$$\therefore I = \frac{E}{R_T} = \frac{20}{2.92} = 6.85A$$

So,

$$I_1 = \frac{I \times R_2}{R_1 + R_2} = \frac{6.85 \times 7}{5 + 7} = \frac{47.95}{12} = 4A$$

$$I_2 = \frac{I \times R_1}{R_1 + R_2} = \frac{6.85 \times 5}{5 + 7} = \frac{34.25}{12} = 2.85A$$


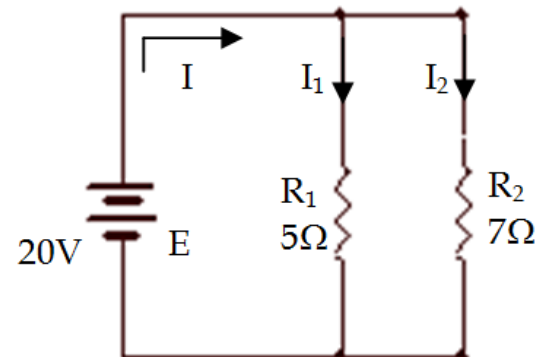


Figure: (b)


Delta-Star transformations

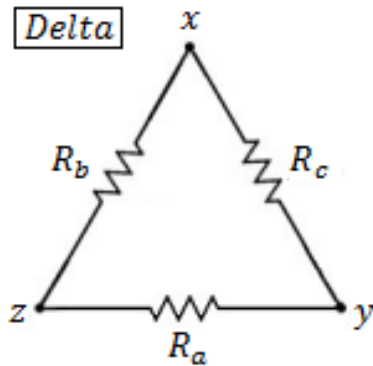

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
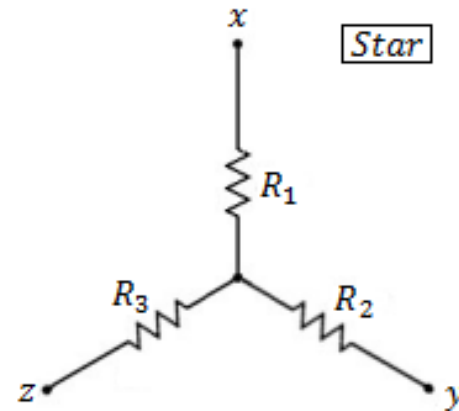
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$



$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Problem 3: Calculate the equivalent resistance of the following circuit shown below,

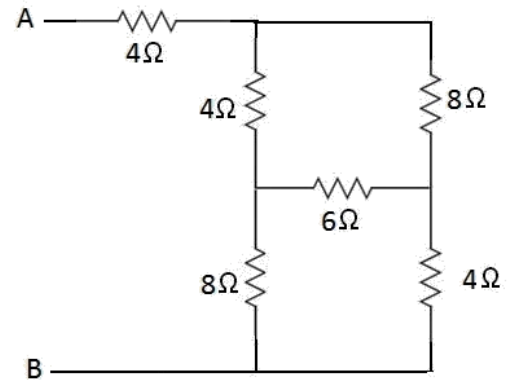

Solution 2:

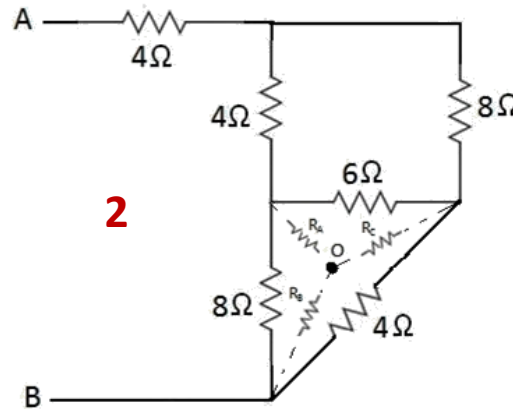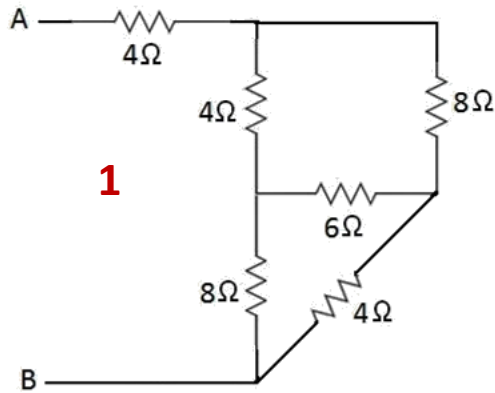

$$R_A = \frac{8 \cdot 6}{8 + 6 + 4}$$

$$R_A = 2.66\Omega$$

$$R_B = \frac{8 \cdot 4}{8 + 6 + 4}$$

$$R_B = 1.77\Omega$$

$$R_C = \frac{6 \cdot 4}{8 + 6 + 4}$$

$$R_C = 1.33\Omega$$

